

Computer Architecture


Tutorial - 07

Answer all questions.

01.

Three resistors $4\ \Omega$, $12\ \Omega$ and $6\ \Omega$ are connected to a supply of 12 V as shown below.

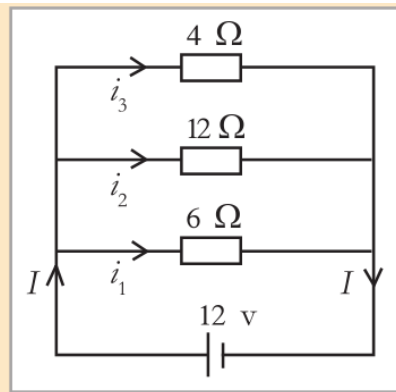- I. Calculate the total resistance of these three resistors.
- II. What current is gained from the electric supply?
- III. Calculate the current flowing through $6\ \Omega$.
- IV. What is the current flowing through $12\ \Omega$?
- V. What is the current flowing through $4\ \Omega$?



02.

Three bulbs B_1 , B_2 and B_3 are connected to 12 V , supply as shown in the following diagram.

- I. Calculate the total resistance of the two bulbs B_2 and B_3 (between Y and Z).
- II. What is the total resistance between the two points X and Z.
- III. What is the current gained from the electric supply.
- IV. Calculate the potential difference between X and Y.
- V. Calculate the potential difference between Y and Z.
- VI. Calculate the current flowing through B_2 bulb.
- VII. Calculate the current through the bulb B_3 .
- VIII. If the bulb B_3 is removed, then what would be the current gain from the electric supply.

